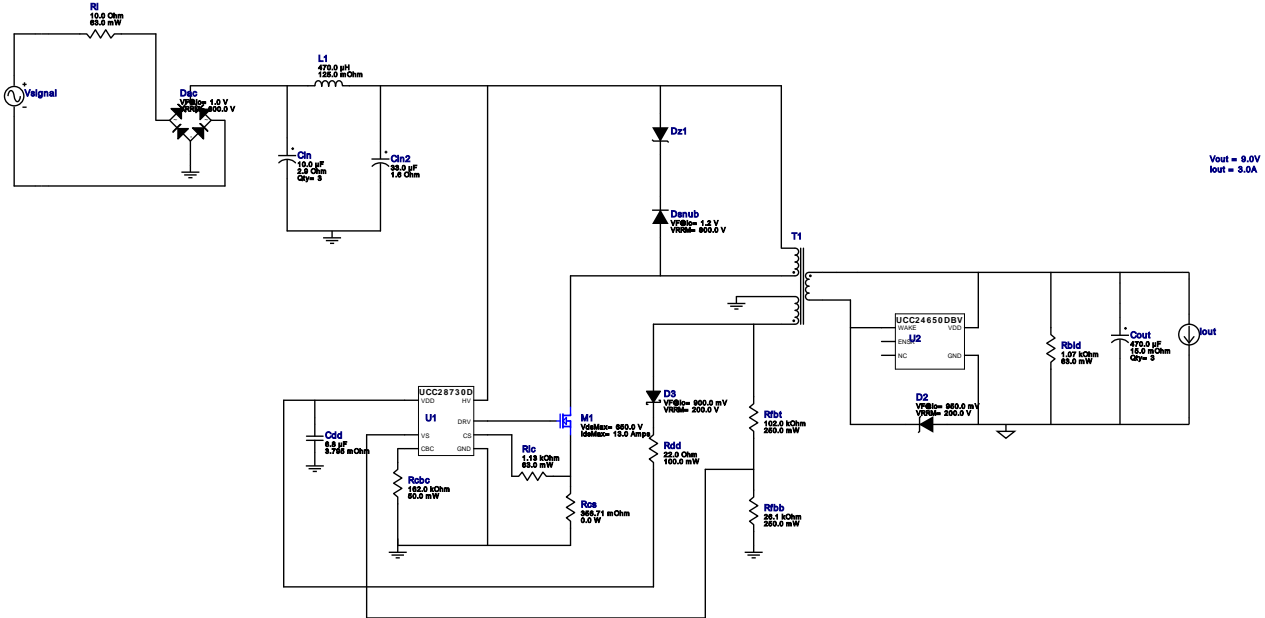


WEBENCH® Design Report

Design : 6 UCC28730DR
UCC28730DR 85V-265V to 20.00V @ 2A

VinMin = 85.0V
VinMax = 265.0V
Vout = 9.0V
Iout = 3.0A

Device = UCC28730DR
Topology = Flyback
Created = 2023-02-16 05:15:05.019
BOM Cost = NA
BOM Count = 26
Total Pd = 8.68W



1. R1bd is a starting point, but may need to be experimented with in order to get minimum current needed to hold Vout at no load. R1c and the feedback resistors may also need adjustment based on the actual transformer used. It is recommended to start this device at light load condition. There is an internal series resistance of 28 kOhms to the CBC pin which sets a maximum cable compensation of a 5V output to 400 mV when CBC is shorted to ground. For more information please click the design assistance button.

2. Click on the transformer symbol and select 'Design Transformer' to design using specific transformer cores and bobbin






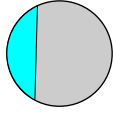
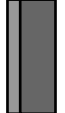







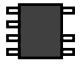
Design Alerts


Component Selection Information







Click on the transformer symbol in the schematic and select "Explore Transformer Core/Bobbin Selection" to design using specific transformer cores and bobbin.







Electrical BOM







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cdd	TDK	C2012X5R1V685K125AC Series= X5R	Cap= 6.8 uF ESR= 3.795 mOhm VDC= 35.0 V IRMS= 3.3493 A	1	\$0.17	0805 7 mm ²
Cin	Kemet	ESG106M400AH4AA Series= 2334	Cap= 10.0 uF ESR= 2.9 Ohm VDC= 400.0 V IRMS= 100.0 mA	3	\$0.29	ESG106 144 mm ²
Cin2	Kemet	PEG124YJ2330QL1 Series= 2394	Cap= 33.0 uF ESR= 1.6 Ohm VDC= 450.0 V IRMS= 306.0 mA	1	\$7.16	PEG124_2000x3700 1008 mm ²







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cout	Kemet	A750MS477M1EAAE015 Series= 3273	Cap= 470.0 uF ESR= 15.0 mOhm VDC= 25.0 V IRMS= 4.9 A	3	\$0.36	 A750_MS 144 mm ²
D2	SMC Diode Solutions	SBRD10200TR	VF@Io= 950.0 mV VRRM= 200.0 V	1	\$0.18	 DPAK 102 mm ²
D3	SMC Diode Solutions	SK220ATR	VF@Io= 900.0 mV VRRM= 200.0 V	1	\$0.06	 SMA 37 mm ²
Dac	Diodes Inc.	HD06-T	VF@Io= 1.0 V VRRM= 600.0 V	1	\$0.15	 MiniDIP 62 mm ²
Dsnub	Microsemi	UFS180JE3/TR13	VF@Io= 1.2 V VRRM= 800.0 V	1	\$0.95	 DO-214BA 42 mm ²
Dz1	Diodes Inc.	SMBJ150A-13-F	Zener	1	\$0.10	 SMB 44 mm ²
L1	MuRata	1447440C	L= 470.0 uH 125.0 mOhm	1	\$2.99	1447440C 1072 mm ²
M1	Infineon Technologies	IPP65R190C7	VdsMax= 650.0 V IdsMax= 13.0 Amps	1	\$2.19	 TO-220AB 79 mm ²
Rbld	Vishay-Dale	CRCW04021K07FKED Series= CRCW..e3	Res= 1.07 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rcs	CUSTOM	CUSTOM Series= ?	Res= 356.71 mOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
Rdd	Yageo	RC0603FR-0722RL Series= ?	Res= 22.0 Ohm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
Rfbb	Vishay-Dale	CMF5026K100FHEB Series= CMF50	Res= 26.1 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.33	 CMF50 46 mm ²
Rfbt	Vishay-Dale	CRCW1206102KFKEA Series= CRCW..e3	Res= 102.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
RI	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rlc	Vishay-Dale	CRCW04021K13FKED Series= CRCW..e3	Res= 1.13 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
T1	Core=TDK , CoilFormer=TDK	Core=B66317G0000X187 , CoilFormer=B66208X1110T001	Lp= 310.0 uH Turns Ratio(Nas)= 10:5 Turns Ratio(Nps)= 42:5 Npri= 42.0 Naux= 10.0 Nsec= 5.0	1	\$0.30	 TDK_B66305 569 mm ²
U1	Texas Instruments	UCC28730DR	Switcher	1	\$0.46	 D0007A 55 mm ²


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U2	Texas Instruments	UCC24650DBVR	Switcher	0	\$0.16	 DBV0005A 15 mm²

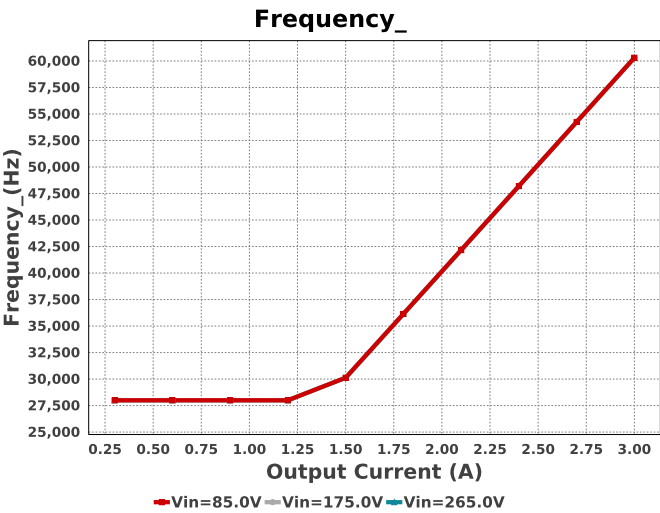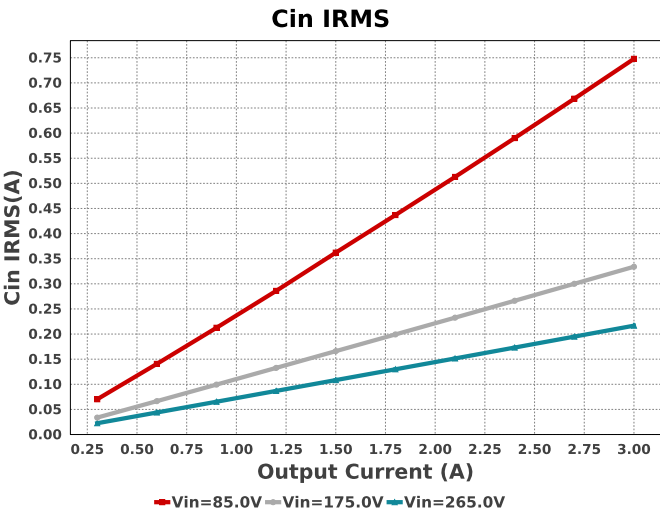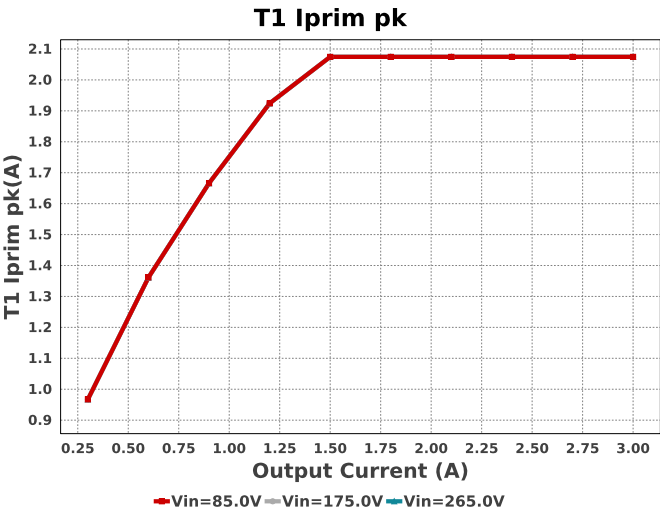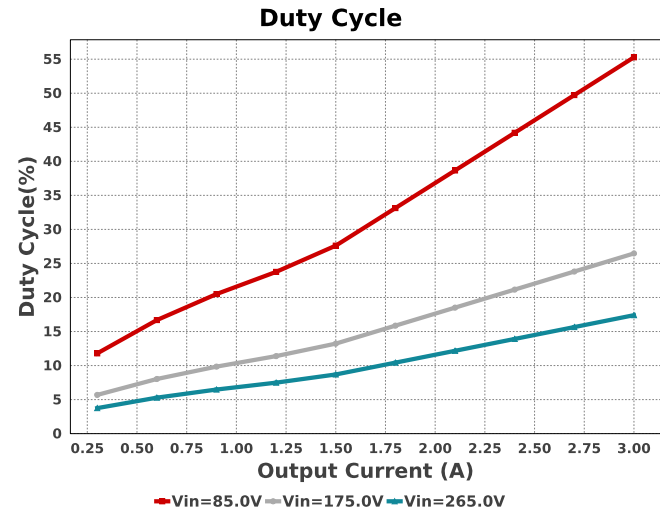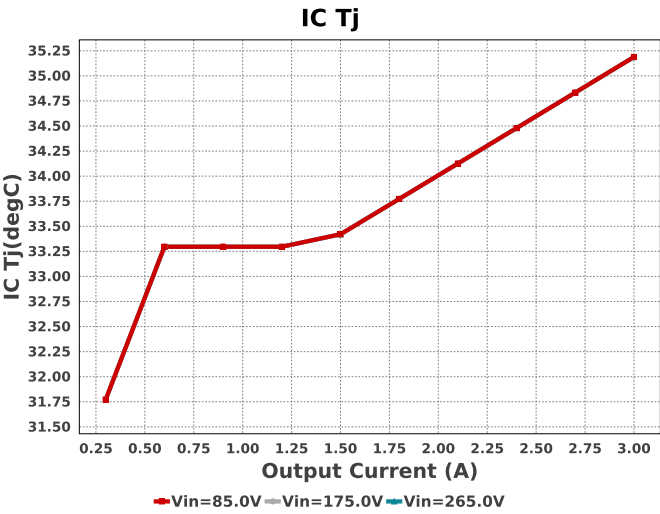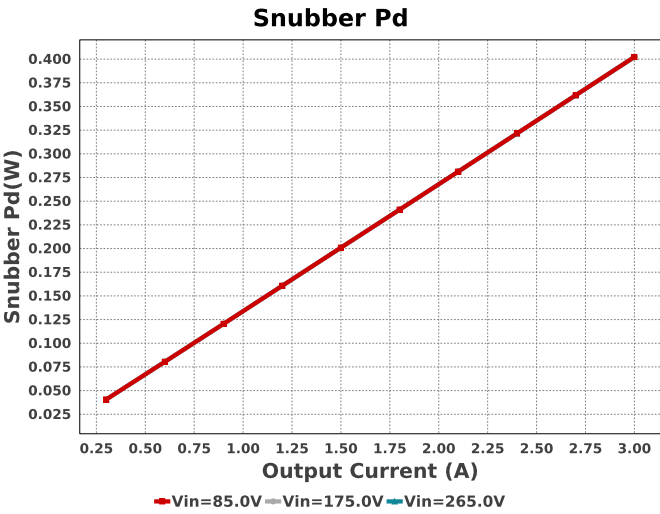

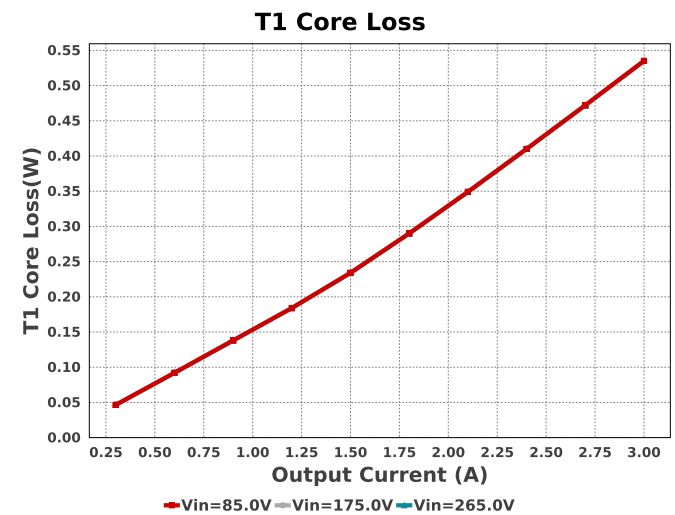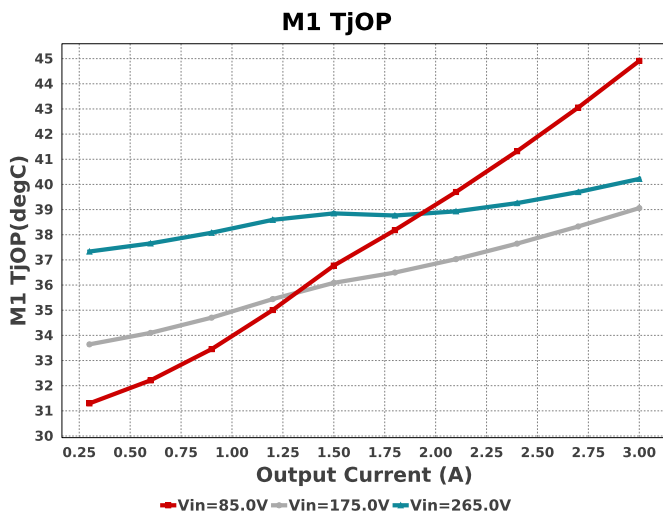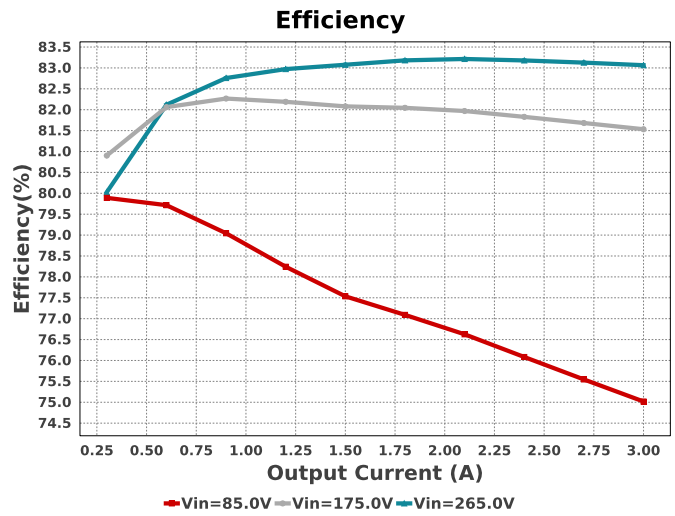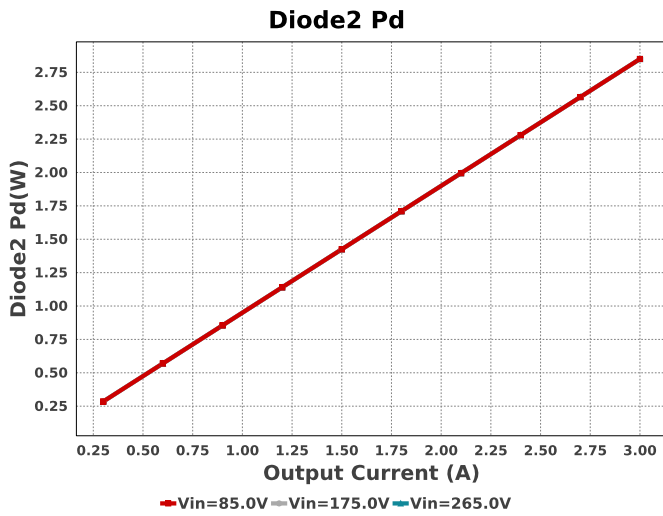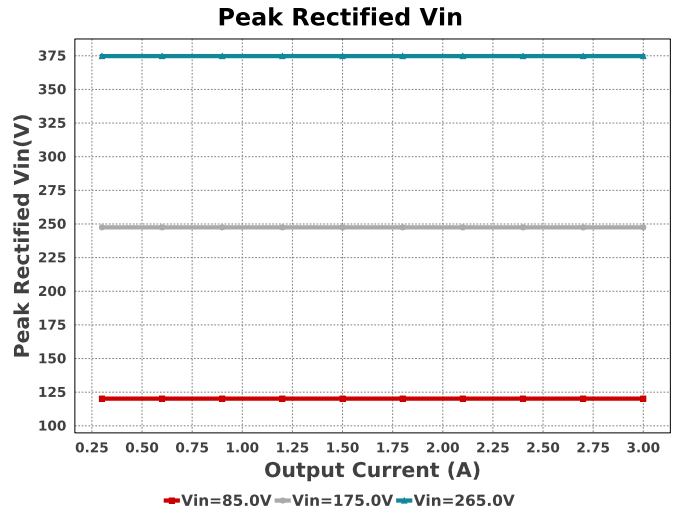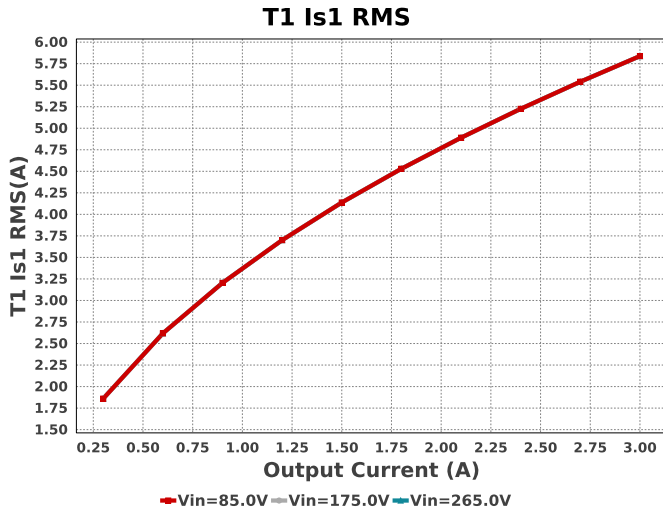

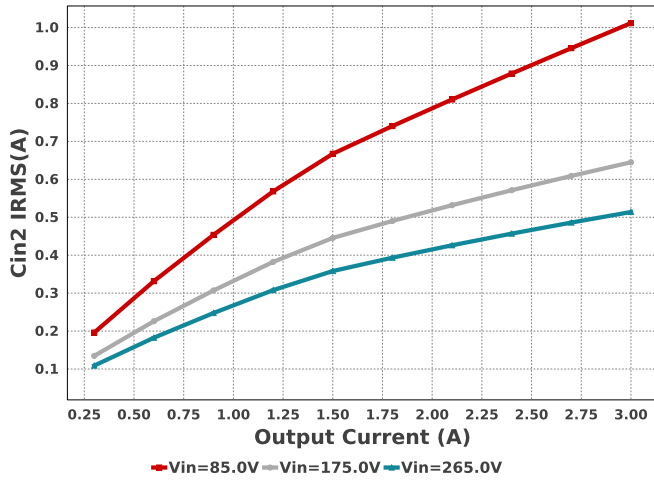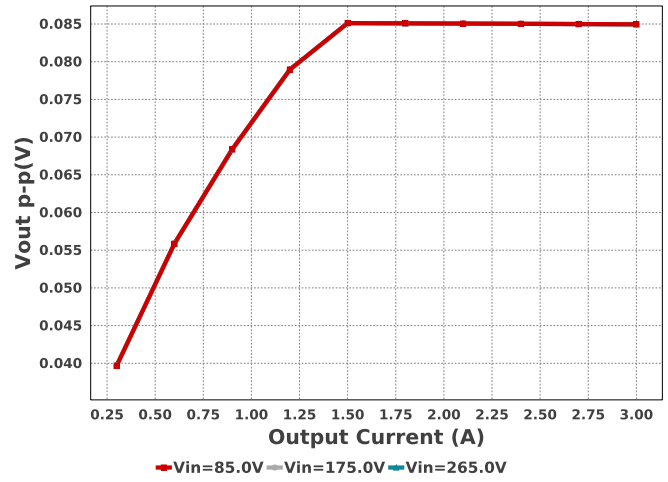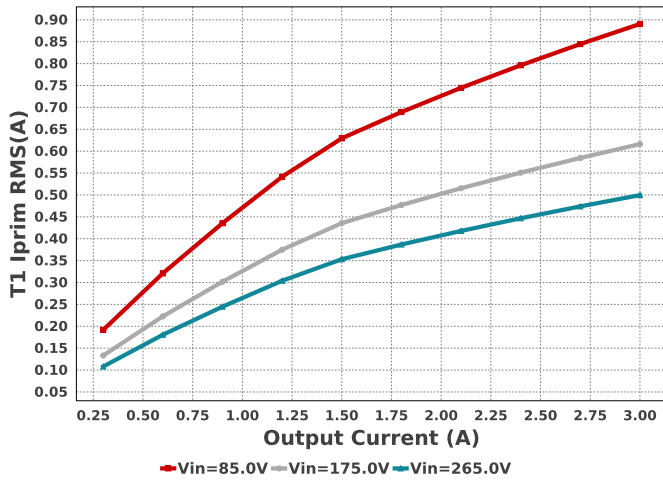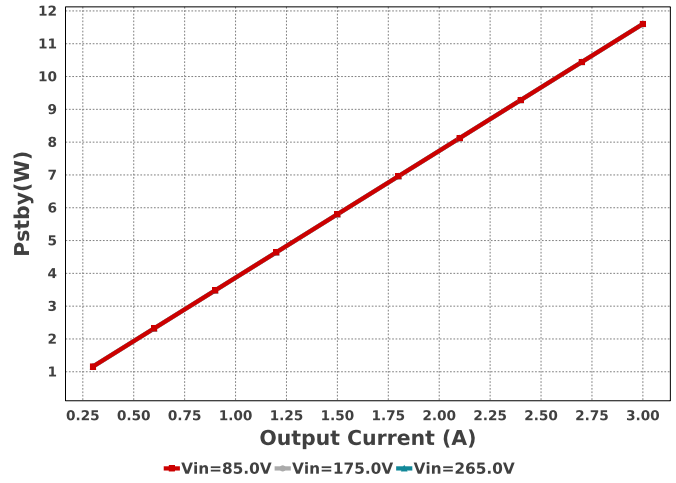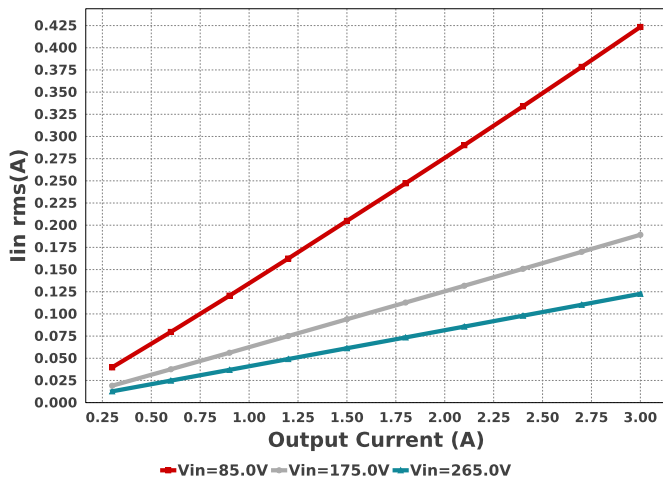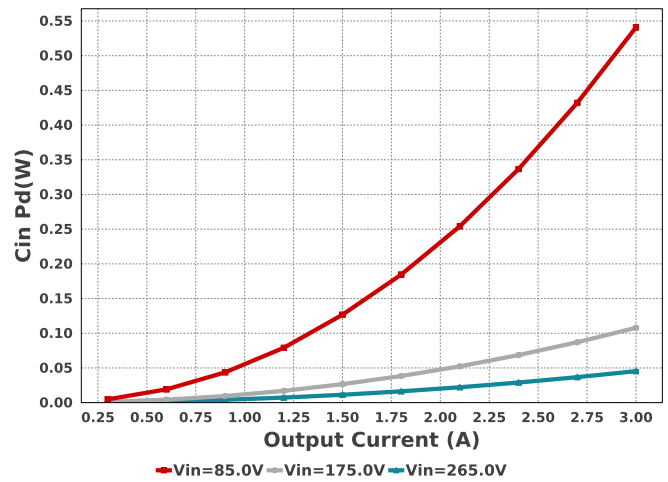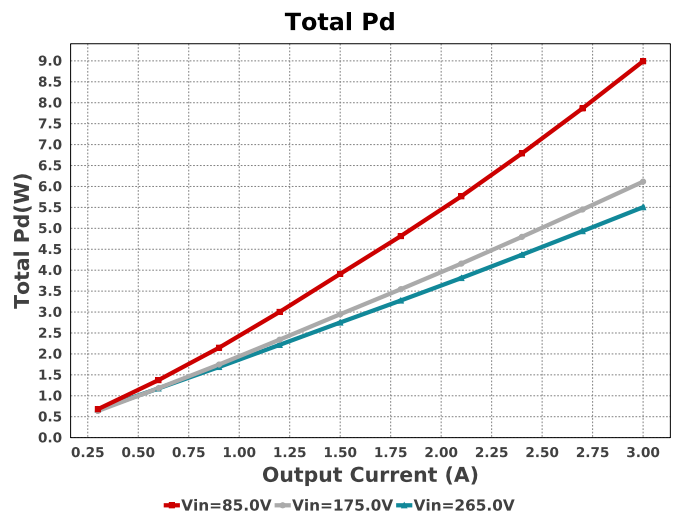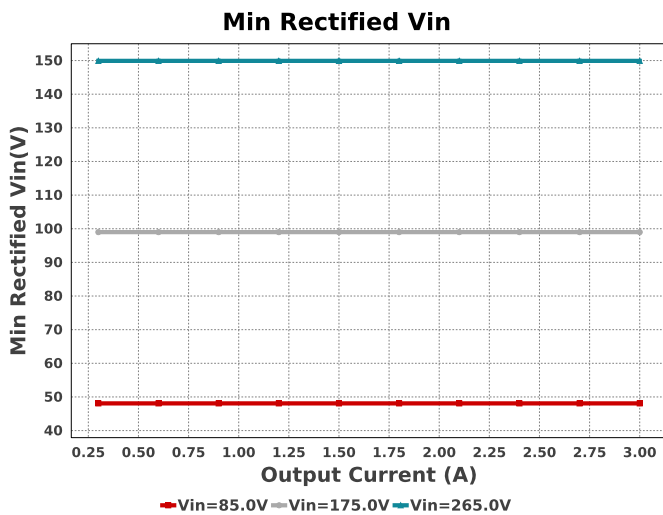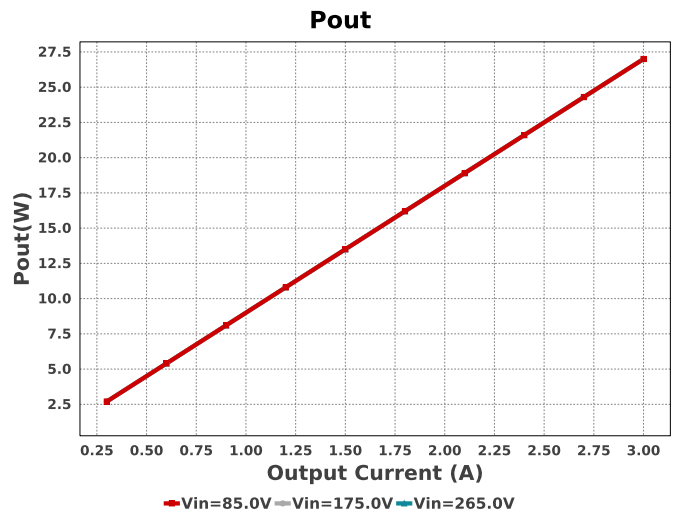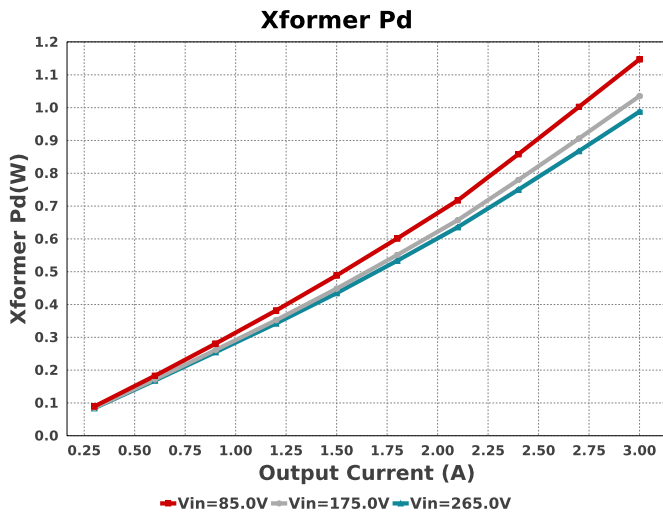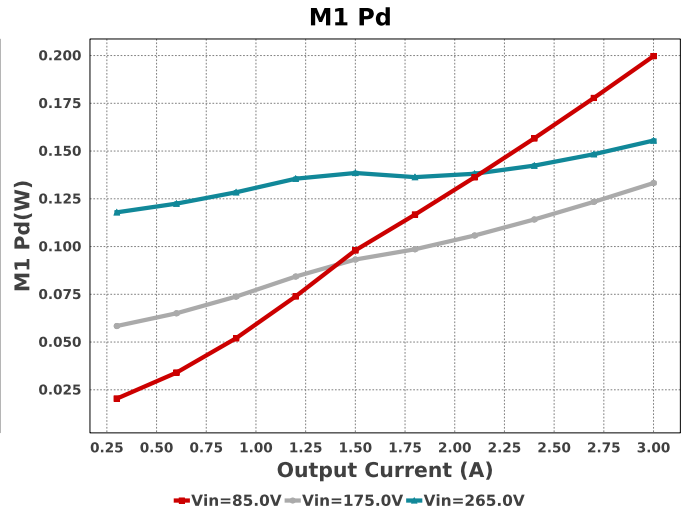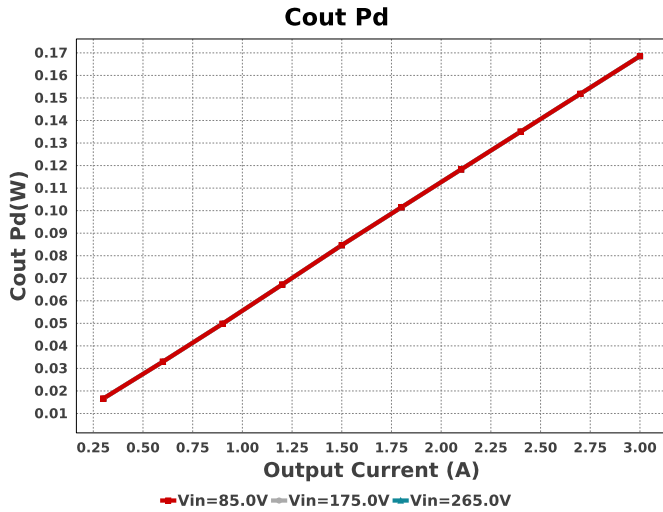Cin2 IRMS**Vout p-p****T1 Iprim RMS****Pstby****Iin rms****Cin Pd**



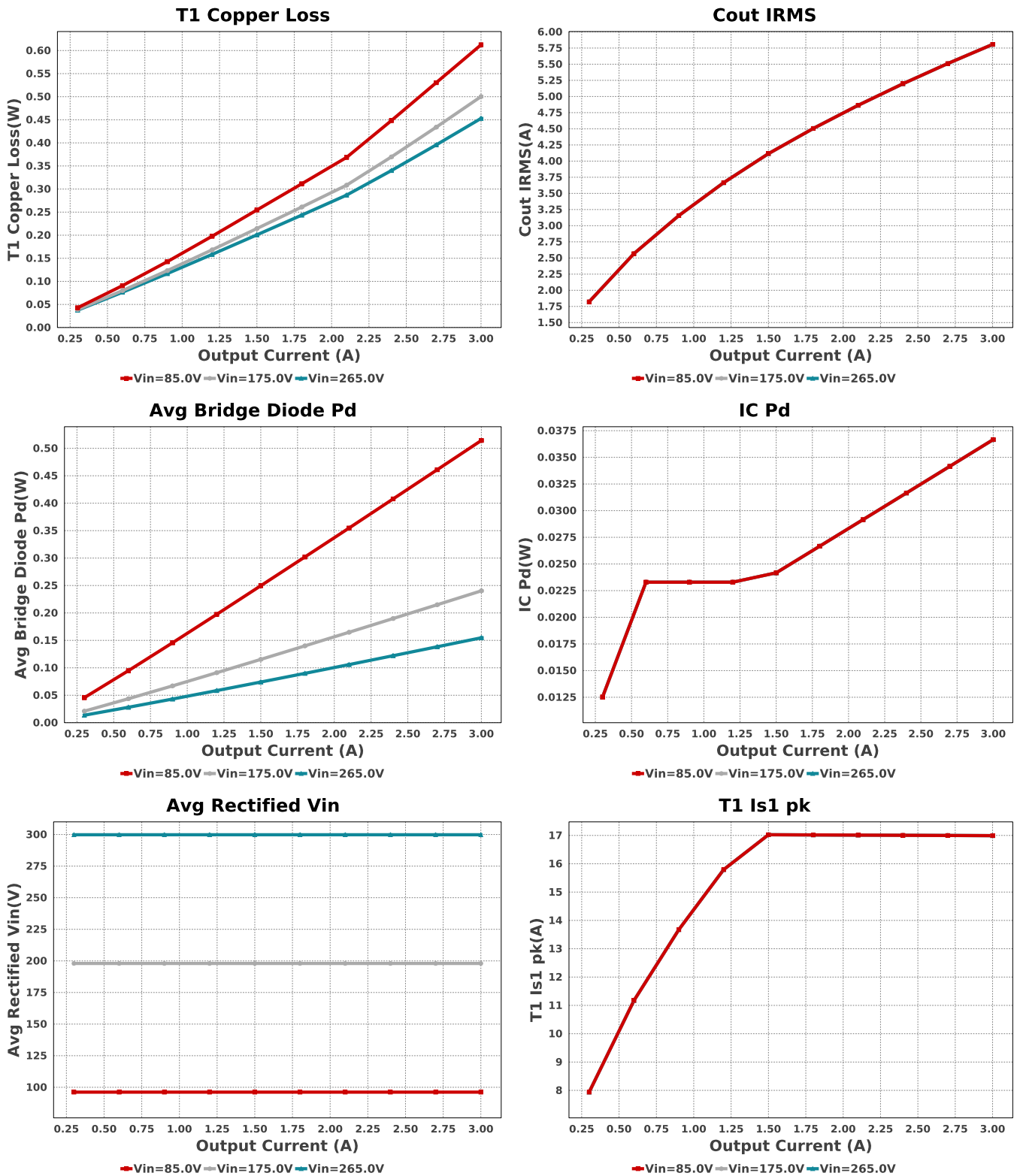

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	741.4 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	531.35 mW	Capacitor	Input capacitor power dissipation
3.	Cin2 IRMS	1.007 A	Capacitor	Input Capacitor Cin2 RMS Ripple Current
4.	Cout IRMS	5.806 A	Capacitor	Output capacitor RMS ripple current
5.	Cout Pd	168.57 mW	Capacitor	Output capacitor power dissipation
6.	Avg Bridge Diode Pd	510.13 mW	Diode	Average Power Dissipation in the Bridge Diode over the AC Line Period
7.	Diode2 Pd	2.85 W	Diode	Diode2 power dissipation
8.	IC Pd	36.665 mW	IC	IC power dissipation
9.	IC Tj	35.188 degC	IC	IC junction temperature
10.	ICThetaJA	141.5 degC/W	IC	IC junction-to-ambient thermal resistance
11.	M1 Pd	199.71 mW	Mosfet	M1 MOSFET total power dissipation

#	Name	Value	Category	Description
12.	M1 TjOP	44.911 degC	Mosfet	M1 MOSFET junction temperature
13.	Avg Bridge Diode Pd	510.13 mW	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
14.	Cin Pd	531.35 mW	Power	Input capacitor power dissipation
15.	Cout Pd	168.57 mW	Power	Output capacitor power dissipation
16.	Diode2 Pd	2.85 W	Power	Diode2 power dissipation
17.	IC Pd	36.665 mW	Power	IC power dissipation
18.	M1 Pd	199.71 mW	Power	M1 MOSFET total power dissipation
19.	Snubber Pd	402.251 mW	Power	Snubber Power Dissipation
20.	T1 Copper Loss	497.01 mW	Power	Transformer Copper Loss Power Dissipation
21.	T1 Core Loss	386.0 mW	Power	Transformer Core Loss Power Dissipation
22.	Total Pd	8.679 W	Power	Total Power Dissipation
23.	Xformer Pd	883.01 mW	Power	Transformer power dissipation
24.	Avg Rectified Vin	96.166 V	System	Average Rectified Voltage for the AC Line Period
			Information	
25.	BOM Count	26	System	Total Design BOM count
			Information	
26.	Duty Cycle	55.28 %	System	Duty cycle
			Information	
27.	Efficiency	75.674 %	System	Steady state efficiency
			Information	
28.	FootPrint	4.018 k mm ²	System	Total Foot Print Area of BOM components
			Information	
29.	Frequency	60.303 kHz	System	Switching frequency
			Information	
30.	Frequency	60.303 kHz	System	Switching frequency
			Information	
31.	Iin rms	419.76 mA	System	RMS Input Current
			Information	
32.	Iout	3.0 A	System	Iout operating point
			Information	
33.	Min Rectified Vin	48.083 V	System	Minimum voltage seen at rectified input
			Information	
34.	Mode	DCM	System	Conduction Mode
			Information	
35.	Peak Rectified Vin	120.207 V	System	Peak voltage seen at rectified input
			Information	
36.	Pout	27.0 W	System	Total output power
			Information	
37.	Total BOM	NA	System	Total BOM Cost
			Information	
38.	Vin_RMS	85.0 V	System	Vin operating point
			Information	
39.	Vout	9.0 V	System	Operational Output Voltage
			Information	
40.	Vout Actual	19.878 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
41.	Vout Tolerance	2.612 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
			Information	
42.	Vout p-p	84.961 mV	System	Peak-to-peak output ripple voltage
			Information	
43.	T1 Copper Loss	497.01 mW	Transformer	Transformer Copper Loss Power Dissipation
44.	T1 Core Loss	386.0 mW	Transformer	Transformer Core Loss Power Dissipation
45.	T1 Iprim RMS	890.509 mA	Transformer	Transformer Primary RMS Current
46.	T1 Iprim pk	2.075 A	Transformer	Transformer Primary Peak Current
47.	T1 Is1 RMS	5.838 A	Transformer	Transformer Secondary1 RMS Current
48.	T1 Is1 pk	16.992 A	Transformer	Transformer Secondary1 Peak Current
49.	Xformer Pd	883.01 mW	Transformer	Transformer power dissipation
50.	Pstby	11.602 W	power	Pstby

Design Inputs

Name	Value	Description
Iout	3.0	Maximum Output Current
VinMax	265.0	Maximum input voltage
VinMin	85.0	Minimum input voltage
Vout	9.0	Output Voltage
acFrequency	60.0	AC Frequency
base_pn	UCC28730	Base Product Number
source	AC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 85.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

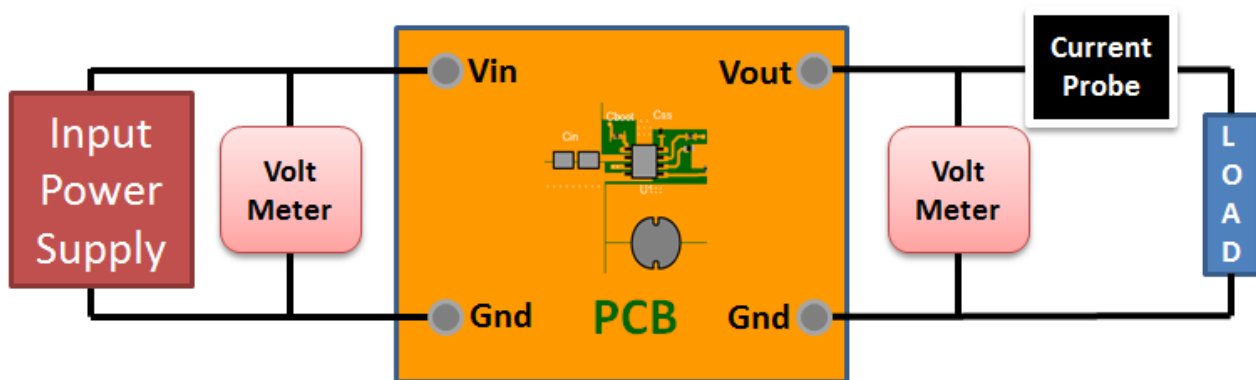

WEBENCH® Transformer Report

#	Name	Value
1.	Core Part Number	B66317G0000X187
2.	Core Manufacturer	TDK
3.	Coil Former Part Number	B66208X1110T001
4.	Coil Former Manufacturer	TDK

Transformer Electrical Diagram

Primary

Turns	42.0
AWG	26.0
Layers	3.0
Strands	2.0
Insulation Type	Heavy Insulated Magnet Wire

Secondary

Turns	5.0
AWG	27.0
Layers	1.0
Strands	4.0
Insulation Type	Triple Insulated

Auxiliary

Turns	10.0
AWG	28.0
Layers	1.0
Strands	4.0
Insulation Type	Heavy Insulated Magnet Wire

Transformer Construction Diagram

Winding Instruction

Winding	AWG	Turns	Winding Orientation
Primary First 2/3.0	26.0	28	Clockwise
Triple Insulated Secondary	27.0	5.0	Counter Clockwise
Auxiliary	28.0	10.0	Counter Clockwise
Primary Second 1/3.0	26.0	14	Clockwise

Transformer Parameters

#	Name	Value
1.	Lpri	3.1E-4H
2.	Inductance Factor(AI)	176.0nH
3.	Npri	42.0
4.	Nsec	5.0
5.	Naux	10.0
6.	Core Type	E25/13/7
7.	Core Material	N87

#	Name	Value
8.	Bmax	0.25T
9.	Switching Frequency	61.65kHz
10.	DMax	0.51
11.	Ipk(Primary)	1.74A
12.	Irms(Primary)	0.72A
13.	Ipk(Secondary)	14.6A
14.	Irms(Secondary)	5.5A

Design Assistance

1. Application Hints: Rbld: Rbld is used to set a minimum load for the circuit, so that in standby the output voltage does not float up. The value chosen by WEBENCH should be a good starting point but may need to be adjusted to achieve minimum power dissipation at standby as well. Rlc: Rlc provides the function of feed-forward line compensation to eliminate change in IPP due to change in di/dt and the propagation delay of the internal comparator and MOSFET turn-off time. For best results the chosen value may need to be adjusted based on board, FET and transformer parasitics. Rfbt & Rfbb: The feedback resistors will set the output voltage of the circuit. The values chosen may need to be fine tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Rwake: To avoid exceeding the maximum source-current rating for WAKE on the UCC24650, a series resistor, Rwake, may be required to limit the WAKE current. For more information regarding Rwake, please refer to the UCC24650 datasheet. Cdd Cdd supplies the device operating current until the output of the converter reaches the target minimum operating voltage. The value calculated by WEBENCH for Cdd is a good starting point since it assumes that the output current of the Flyback is available to charge the output capacitance until the minimum output voltage is achieved, but may need to be adjusted. Part Description: The UCC28730 family of flyback power supply controllers provides Constant-Voltage (CV) and Constant-Current (CC) output regulation. Primary-Side Regulation (PSR) eliminates the use of an Opto-Coupler. The UCC24650 is an easy to use secondary-side voltage monitor that can provide a wake-up alert signal to a primary-side regulation (PSR) controller, such as the UCC28730, to help achieve <5mW Zero-Power standby loss in many applications and provide excellent load transient performance. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/ucc28730.pdf> <http://www.ti.com/lit/ds/symlink/ucc24650.pdf>

2. Master key : 5601E6D956368EA766F626A92E56EDD0[v1]

3. **UCC28730 Product Folder** : <http://www.ti.com/product/UCC28730> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.